

Lecture 7 – Capacitors, RC Networks, Step Response

February 27, 2020

Contents:

1. Capacitor: a quick review
2. Differentiator (from Tuesday)
3. Analysis of RC circuits

Reading Assignment:

Agarwal and Lang, Ch. 9 (§ 9.1.1, 9.2.1, 9.3.1), 10 (§ 10.1)


Handouts:

Lecture 7 notes

Quiz 1 on March 11th. It covers everything until today (including pssets!)

1. Capacitor: a quick review

- Ideal parallel-plate capacitor:

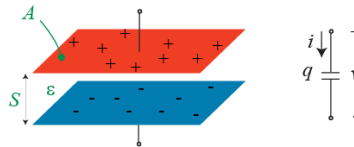

- Relationship between charge in plates and voltage across capacitor [from Gauss' law]:

$$q = Cv$$

Units:

$$\text{Coulombs} = \text{Farads} \times \text{Volts}$$

In parallel plate capacitor:

$$C = \epsilon \frac{A}{S}$$

With:

$$\epsilon = \text{permittivity [F/cm]}$$

Device equation for capacitor





$$q = Cv$$

Current is rate of flow of charge:

$$i = \frac{dq}{dt}$$


Therefore, in a capacitor:

$$i = C \frac{dv}{dt}$$

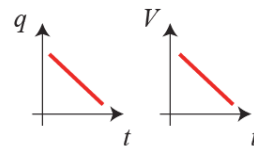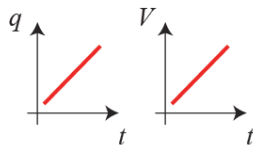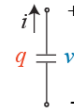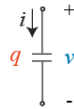


2. Differentiator (from last lecture)

This is what we want:

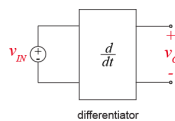

Could use a capacitor:

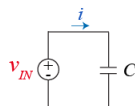


where:

$$i = C \frac{dv_{IN}}{dt}$$

– For differentiator, need to convert i into v_O

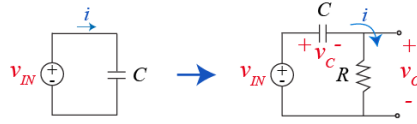- Differentiator: use small resistance to transform i into v_O :



Want:

$$i = C \frac{dv_C}{dt} \simeq C \frac{dv_{IN}}{dt}$$

so that:

$$v_O = iR \simeq RC \frac{dv_{IN}}{dt}$$

This requires:

$$v_O \ll v_C \simeq v_{IN}$$

Or:


$$RC \frac{dv_{IN}}{dt} \ll v_{IN}$$

Signal time derivative can't be too high \rightarrow upper limit to frequency content of signal


Op-amps to the rescue...

$i \rightarrow v$ and $v \rightarrow i$ transformation


Remember this configuration:

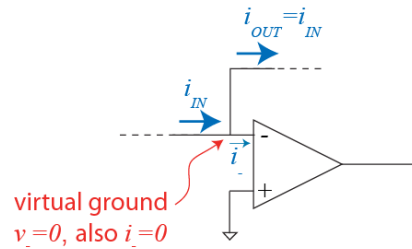

Voltage-to-current converter:

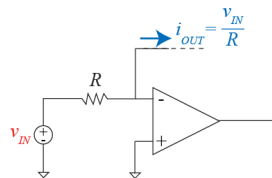


Current-to-voltage converter:

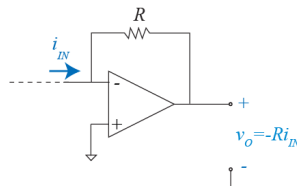

Op-amp differentiator

Use an op-amp i-v converter:

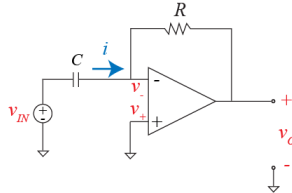

Inverting input is virtual ground:

$$v_+ = 0 \rightarrow v_- \simeq 0$$

Then


$$i \simeq C \frac{dv_{IN}}{dt}$$

At output:

$$v_O = -iR$$

All together:

$$v_O \simeq -RC \frac{dv_{IN}}{dt}$$

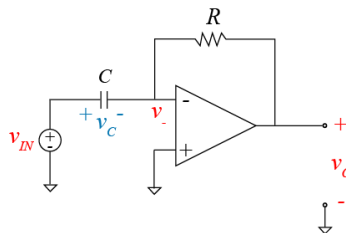

Differentiator is accurate if:

$$v_C \simeq v_{IN}$$

which requires:

$$|v_-| \ll v_{IN}$$

v_- is given by:

$$v_+ - v_- = \frac{v_O}{A} \rightarrow v_- = -\frac{v_O}{A} = -\frac{RC}{A} \frac{dv_{IN}}{dt}$$

We need now:


$$\left| \frac{RC}{A} \frac{dv_{IN}}{dt} \right| \ll v_{IN} \quad \leftarrow \text{Bandwidth of differentiator greatly improved!}$$

Coming back to capacitors...

- Another way to write capacitor equation:

$$i = C \frac{dv}{dt} \rightarrow v = \frac{1}{C} \int_{-\infty}^t i dt$$

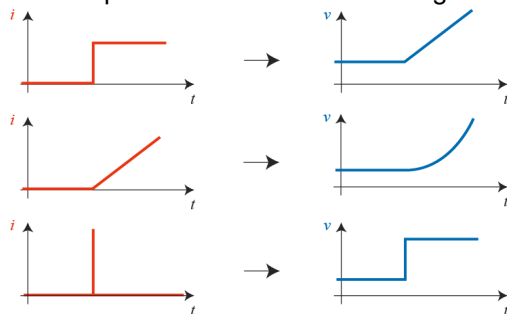- Relationship between current and voltage:



We need initial conditions to fully define the state of the capacitor

Abrupt change in voltage gives rise to infinite current!
→ Not possible in real circuits!

Voltage across capacitor depends on the entire past history of current flowing through it → memory!

Power and energy in a capacitor

- Power is rate of flow of energy. For capacitor:

$$p = vi = vC \frac{dv}{dt} = \frac{d}{dt} \left(\frac{1}{2} C v^2 \right) = \frac{dw_E}{dt}$$

- If $dv^2/dt > 0 \rightarrow p > 0$: energy being dumped into C
- If $dv^2/dt < 0 \rightarrow p < 0$: energy being removed from C

- Unlike resistor, capacitor stores energy (in electrostatic form).
- Electrostatic energy stored in capacitor:


$$w_E = \frac{1}{2} C v^2$$

- Capacitors can store substantial amounts of energy!



Capacitors are everywhere...

Doppler Ultrasound System

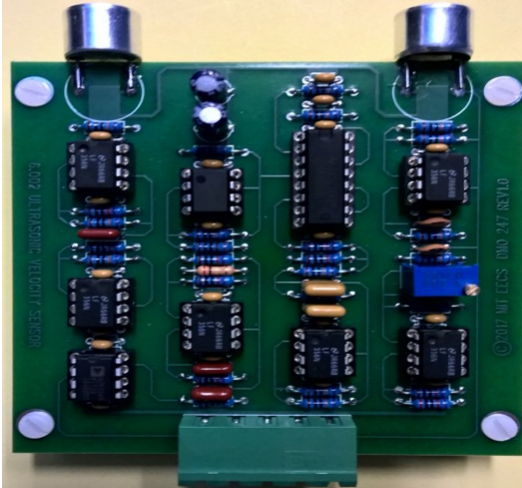


6.002 Spring 2020


13

Capacitors are there, even when you don't see them...

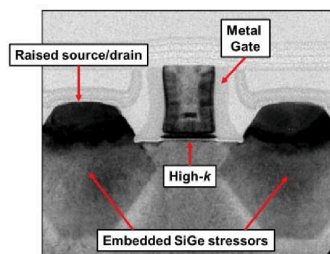- Transistors (MOSFETs) really looks like:



Intel's 32 nm MOSFET

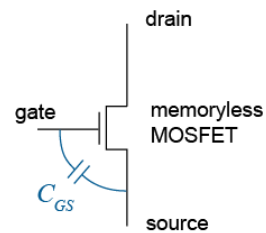

- The Capacitance between the gate and the source is key to give the transistor its ability to control current flow (and its time response).
- All other devices have capacitance associated with them.

→ **Need to understand impact of capacitors on circuit operation**


6.002 Spring 2020

Lecture 7

14

3. Analysis of RC circuits

- Consider the following circuit:

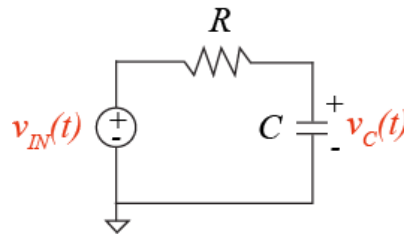

- Circuit behavior completely determined by:
 - Differential equation describing circuit
 - Input waveforms
 - Initial conditions



- Consider example with:

- Input step function: $v_{IN}(t) = V_{IN} u_o(t)$
- Initial condition: $v_C(t=0) = 0$




- How does $v_C(t)$ evolve in time?

- First, think physics!

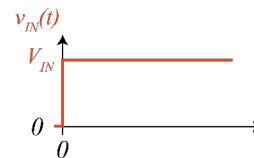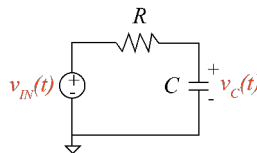

- Situation at $t=0^-$:

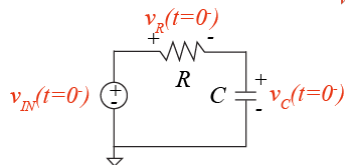

$$v_C(t=0^-) = 0$$

At $t=0^-$:

$$v_{IN}(t = 0^-) = 0$$

$$v_C(t = 0^-) = 0$$


Since KVL demands that:

$$v_{IN} = v_R + v_C$$

Then:

$$v_R(t = 0^-) = 0$$

- Situation at $t=0^+$:

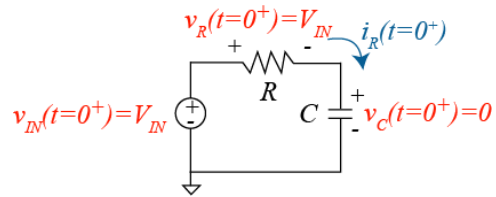

Capacitor can't change voltage abruptly:

$$v_C(t = 0^+) = 0$$

V_{IN} appears across R :


$$v_R(t = 0^+) = V_{IN}$$

Resistor current:

$$i_R(t = 0^+) = \frac{V_{IN}}{R}$$

i_R starts charging C :

$$\left. \frac{dv_C}{dt} \right|_{t=0^+} > 0$$

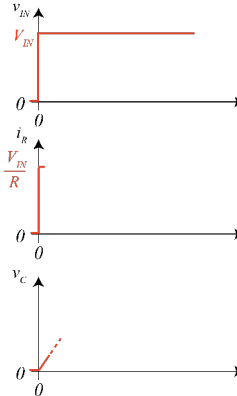


6.002 Spring 2020

Lecture 7

19

- Situation at $t=\infty$:

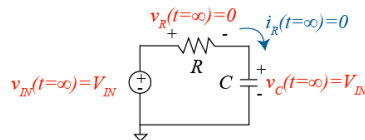

Capacitor will charge until it reaches the maximum voltage possible, V_{IN} :

$$v_C(t = \infty) = V_{IN}$$

No voltage across R :


$$v_R(t = \infty) = 0$$

Resistor current is zero:

$$i_R(t = \infty) = 0$$

Nothing changes from here on:

→ *steady-state condition*


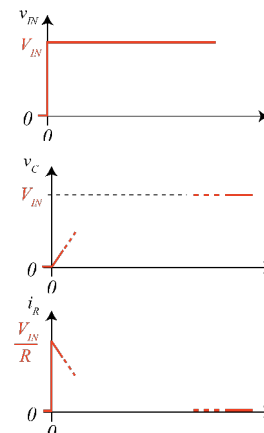


6.002 Spring 2020

Lecture 7

20

- Solution roughly looks like:

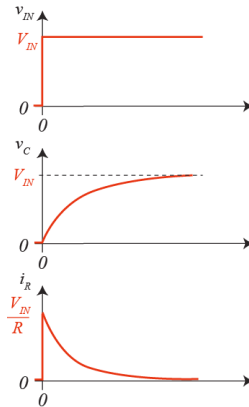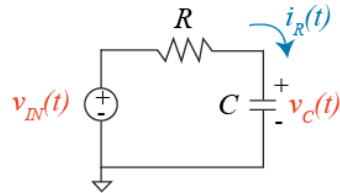

- Features of solution:
 - Increase of $v_C(t)$ slows down with time
 - Given enough time, $v_C(t)$ saturates
 - $i_R(t)$ peaks at $t=0^+$ and drops from there to eventually zero
- What is the detailed shape? How long does it take for steady-state to be achieved? → need to solve problem mathematically



6.002 Spring 2020

Lecture 7

21

Mathematical solution (18.03 to the rescue!)

- Given:

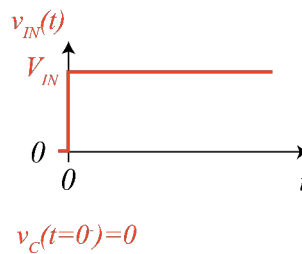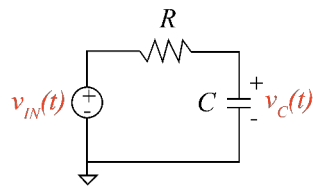

- Want $v_C(t)$

- Steps:



1. Formulate differential equation
2. Find particular solution
3. Find homogeneous solution
4. Apply initial conditions

6.002 Spring 2020

Lecture 7

22

1. Formulate differential equation:

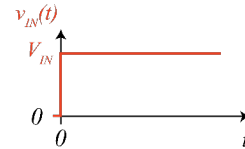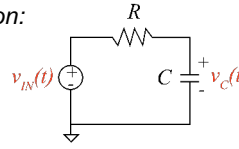

$$v_C(t=0) = 0$$

One node analysis.

Node equation for $v_C(t)$:

$$\frac{v_C(t) - v_{IN}(t)}{R} + C \frac{dv_C(t)}{dt} = 0$$

Rearrange:

$$RC \frac{dv_C(t)}{dt} + v_C(t) = v_{IN}(t)$$

Solution of form:

$$v_C(t) = v_{CH}(t) + v_{CP}(t)$$

Homogeneous solution
("natural response")

Particular solution
("forced response")

2. Find particular solution:

Interested in solution for $t > 0$. In this range:

$$v_{IN}(t) = V_{IN}$$

Differential equation becomes:

$$RC \frac{dv_C(t)}{dt} + v_C(t) = V_{IN}$$

Particular solution satisfies differential equation:

$$RC \frac{dv_{CP}(t)}{dt} + v_{CP}(t) = V_{IN}$$

Try solution of form:

$$v_{CP}(t) = K$$

Then:

$$v_{CP}(t) = V_{IN}$$

3. Find homogeneous solution

Homogeneous differential equation:

$$RC \frac{dv_{CH}(t)}{dt} + v_{CH}(t) = 0$$

Solution of the form:

$$v_{CH}(t) = Ae^{-\frac{t}{\tau}}$$

Value of τ that satisfies differential equation:

$$\tau = RC$$

Then:

$$v_{CH}(t) = Ae^{-\frac{t}{RC}}$$

4. Apply initial conditions

Total solution so far:

$$v_C(t) = V_{IN} + Ae^{-\frac{t}{RC}}$$

Initial condition:

$$v_C(0) = 0$$

[voltage across capacitor can't change abruptly]


Then:

$$A = -V_{IN}$$




Final solution:

$$v_C(t) = V_{IN}(1 - e^{-\frac{t}{RC}})$$

- Can also compute current through R:

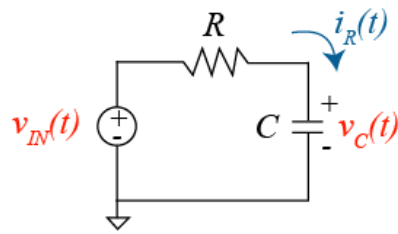
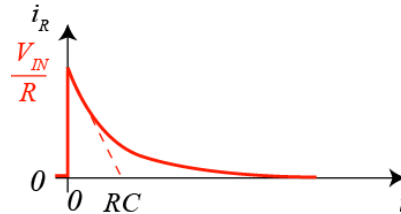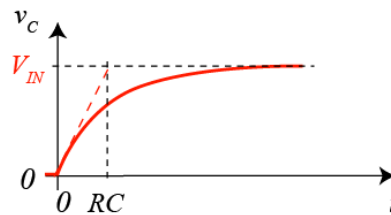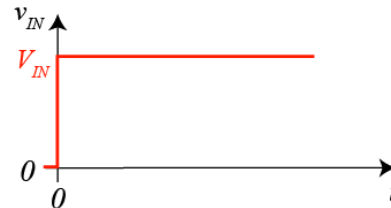
$$i_R(t) = \frac{v_{IN}(t) - v_C(t)}{R} = \frac{V_{IN}}{R} e^{-\frac{t}{RC}}$$



6.002 Spring 2020

Lecture 7

27

Summary

- Capacitors are everywhere... (even when you don't see them)
- Circuits with capacitors exhibit memory: voltage across capacitor depends on the entire past history of current flowing through it.
- A MOSFET has capacitance associated with its gate.
- Device equation for capacitor:

$$i = C \frac{dv}{dt}$$

- Capacitors can store energy.
- RC circuits characterized by first-order linear differential equation.
- Time constant of RC circuits: $\tau = RC$.

6.002 Spring 2020

Lecture 7

28