

6.002 CIRCUITS AND ELECTRONICS

Lecture 22 – Amplifier biasing and small-signal analysis

May 5, 2020

Contents:

1. Review of MOSFET
2. MOSFET amplifier (cont.)
3. Small-signal analysis
4. Amplifier biasing

Reading Assignment:

Agarwal and Lang, Ch. 7 (§ 7.7-7.9), Ch. 8 (§ 8.1, 8.2)

Handouts:



Lecture 22 notes

Announcements:

This lecture is being recorded and it will be posted in the certificates-protected part of the 6.002 website

1. Review of MOSFET

- MOSFET output characteristics

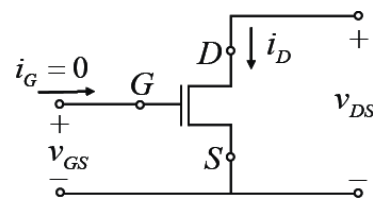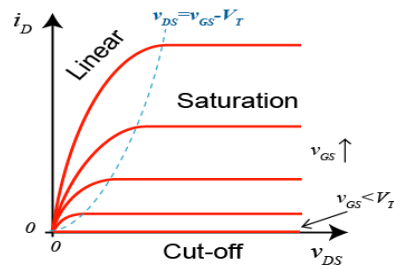

- **Cut-off:** $v_{GS} \leq V_T$

$$i_D = 0$$


- **Linear or triode:** $v_{GS} > V_T, v_{DS} \leq v_{GS} - V_T$

$$i_D = K(v_{GS} - V_T - \frac{v_{DS}}{2})v_{DS}$$


- **Saturation:** $v_{GS} > V_T, v_{DS} \geq v_{GS} - V_T$

$$i_D = \frac{K}{2}(v_{GS} - V_T)^2$$


- MOSFET model for amplification:

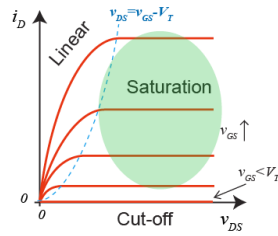


- Equivalent circuit model:

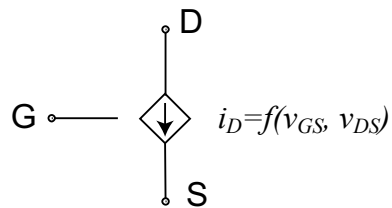



2. MOSFET amplifier (cont.)


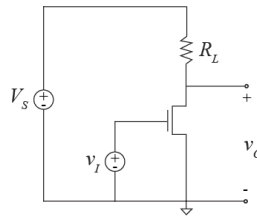


Load diagram:

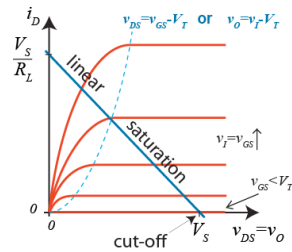

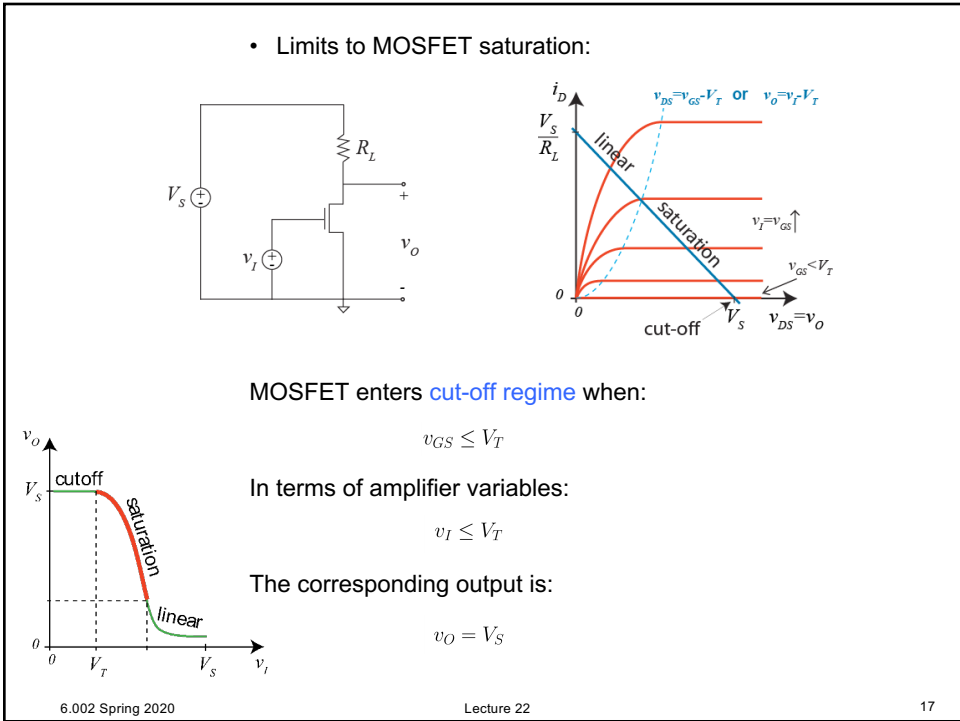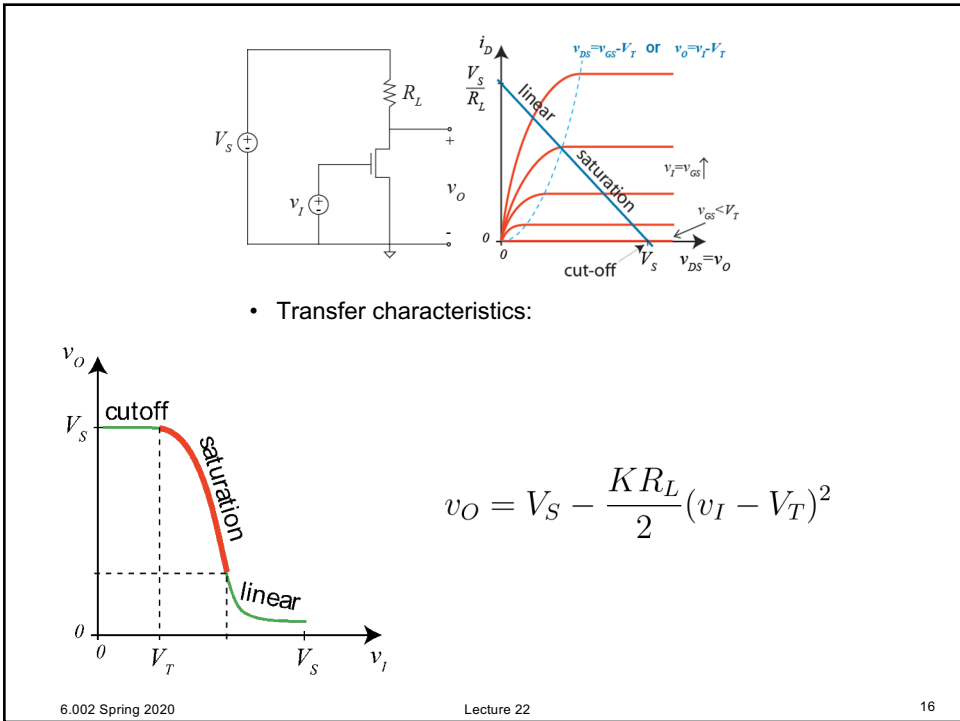For proper operation, MOSFET must be biased in saturation.



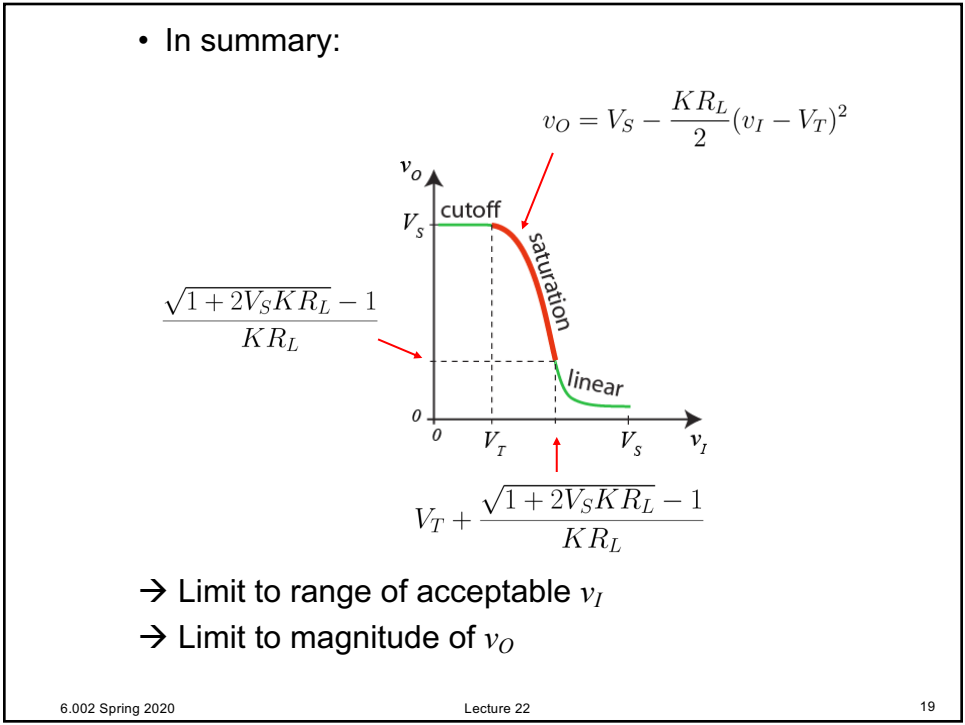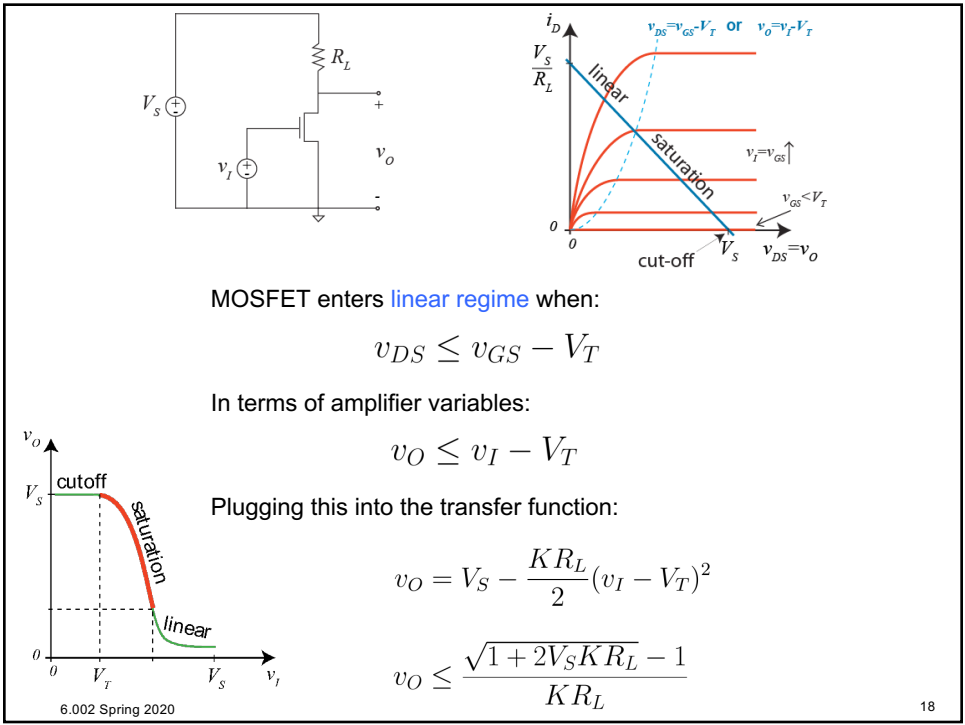


3. Small-signal analysis

- Transfer characteristics of MOSFET amplifier are not linear:

$$v_O = V_S - \frac{KR_L}{2}(v_I - V_T)^2$$

→ distortion!

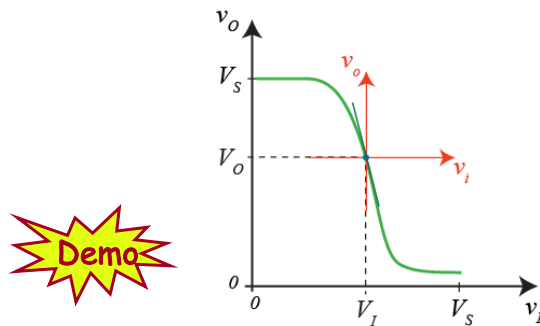- Key insight: if magnitude of signal is *small* relative to V_S , transfer characteristics around bias point look fairly *linear* → low distortion.



6.002 Spring 2020

Lecture 22

21

- If one can linearize, what are the v_o - v_i small-signal transfer characteristics?

- Large-signal transfer characteristics:

$$v_O = V_S - \frac{KR_L}{2}(v_I - V_T)^2$$

- Input is of form:

$$v_I = V_I + v_i$$

- Output should then be of form:

$$\begin{aligned} v_O &= V_O + v_o = V_S - \frac{KR_L}{2}(V_I + v_i - V_T)^2 \\ &= V_S - \frac{KR_L}{2}[(V_I - V_T)^2 + 2v_i(V_I - V_T) + v_i^2] \\ &= V_S - \frac{KR_L}{2}(V_I - V_T)^2 - KR_L(V_I - V_T)v_i - \frac{KR_L}{2}v_i^2 \end{aligned}$$

- Identify terms:

– Bias terms:

$$V_O = V_S - \frac{KR_L}{2}(V_I - V_T)^2$$

– Small-signal terms:

$$v_o = -KR_L(V_I - V_T)v_i - \frac{KR_L}{2}v_i^2$$

6.002 Spring 2020

Lecture 22

22

- Small-signal terms:


$$v_o = -KR_L(V_I - V_T)v_i - \frac{KR_L}{2}v_i^2$$

- Linearizing means keeping only the linear term:

$$v_o \simeq -KR_L(V_I - V_T)v_i$$

- Small-signal gain:
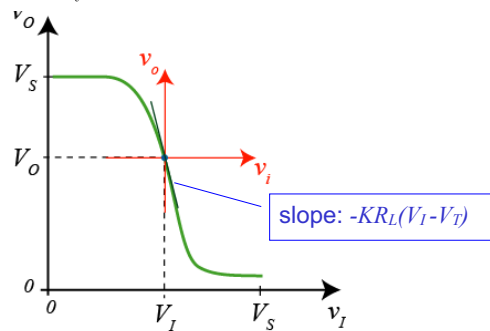
$$A_v = \frac{v_o}{v_i} \simeq -KR_L(V_I - V_T)$$



6.002 Spring 2020

Lecture 22

23

$$v_o = -KR_L(V_I - V_T)v_i - \frac{KR_L}{2}v_i^2$$

$$v_o \simeq -KR_L(V_I - V_T)v_i$$

- When is this approximation good?


quadratic term \ll *linear term*

$$\frac{KR_L}{2}v_i^2 \ll KR_L(V_I - V_T)v_i$$

Or:

$$v_i \ll 2(V_I - V_T)$$

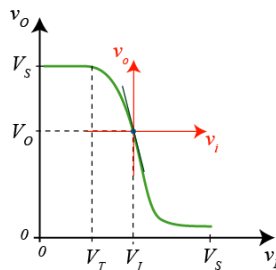- The higher the bias, the easier it is to deliver this condition.




6.002 Spring 2020

Lecture 22

24

- Let's put some numbers: use 2N7000 ($V_T=1.8\text{ V}$, $K=0.1\text{ A/V}^2$) with $R_L=1\text{ k}\Omega$ and $V_S=5\text{ V}$.

Transfer characteristics look like:

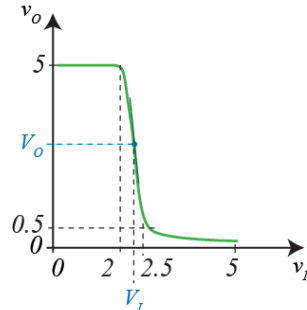

If select $V_o=2.6\text{ V}$, then $V_I=2.2\text{ V}$, and:

$$\left| \frac{v_o}{v_i} \right| \simeq -K R_L (V_I - V_T) \sim 40$$

This is true as long as:

$$v_i \ll 2(V_I - V_T)$$

- More generally, obtain small-signal transfer characteristics by **Taylor series expansion of large-signal transfer characteristics**.
- If large-signal transfer characteristics are:

$$v_O = f(v_I)$$

- Then, if $v_I = V_I + v_i$, expand around (V_I, V_O) :

$$v_O = V_O + v_o = f(V_I + v_i) \simeq f(V_I) + \left. \frac{df}{dv_I} \right|_{V_I} v_i$$

- Small-signal transfer characteristics are:

$$v_o = \left. \frac{df}{dv_I} \right|_{V_I} v_i$$

- And small-signal gain is:

$$\frac{v_o}{v_i} = \left. \frac{df}{dv_I} \right|_{V_I}$$

[check that from here, you get the same result as above]

4. Amplifier biasing

- To have signal entirely within acceptable v_I range, apply signal, v_i , on top of bias, V_I :


Remember notation:

$$v_I(t) = V_I + v_i(t)$$

total bias small signal

$$v_i(t) = V_i \sin \omega t$$

amplitude

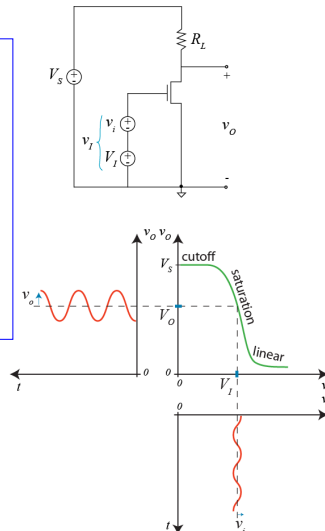


6.002 Spring 2020


Lecture 22

27

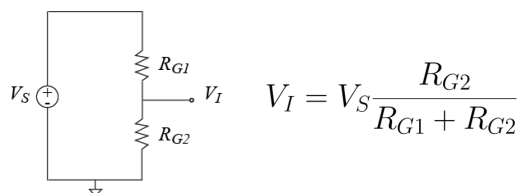- Problem: need two power supplies, V_S and V_I
- But, can produce V_I out of V_S using voltage divider!



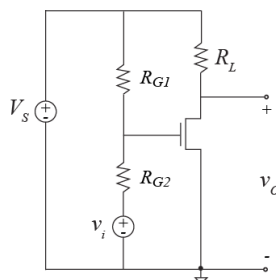- And connecting everything to the circuit:




6.002 Spring 2020

Lecture 22


28

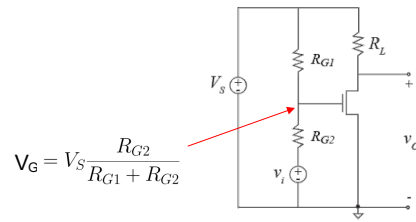- Resistor values have to be designed correctly to bias MOSFET in saturation




input bias too low

input bias too high

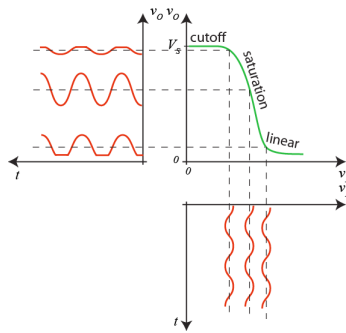

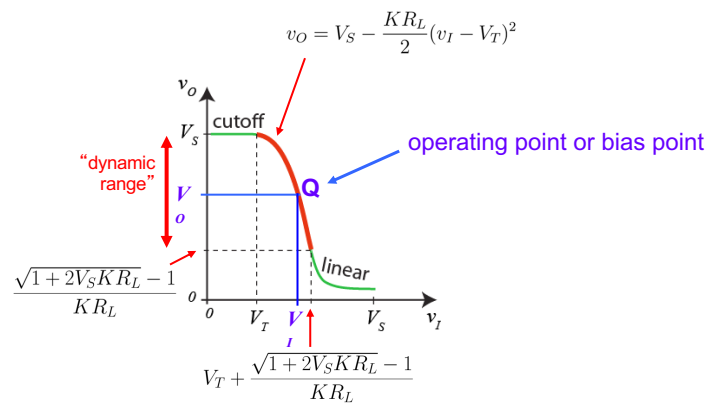- What is a good choice for operating point?
→ Close to middle of the range of acceptable output!



Notice: non-linear transfer characteristics

→ middle of the range of v_o does not correspond to middle of range of v_i

Summary

- To ensure MOSFET operation in the saturation regime, apply bias to the input signal.
- Even if transfer characteristics are non linear, adequate amplifier operation can be obtained for signals of small amplitude.
- For small signals, calculate amplifier gain by linearizing large-signal transfer characteristics of amplifier at bias point.
- In general, this is done by selecting linear term in Taylor series expansion of transfer characteristics around bias point.