

## 6.002 CIRCUITS AND ELECTRONICS

### Lecture 24 – Three transistors amplifier... Let's make an op-amp!

May 12, 2020

#### Contents:

1. Differential amplifier: motivation
2. MOSFET differential amplifier
3. Amplifier biasing
4. Beyond 6.002

#### Reading Assignment:

Agarwal and Lang, Ch. 7 (examples 7.19-7.22), Ch. 8 (example 8.3)

#### Handouts:

Lecture 24 notes

#### Announcements:

- Final exam (5/18 in Gradescope) will focus on sinusoidal steady state and non-linear devices, however it will build up on all the other topics of 6.002, so please review the content of all psets and quizzes.
- This lecture is being recorded and it will be posted in the certificates-protected part of the 6.002 website.
- Voluntary (not graded) HW 10 can be found in website.


6.002 Spring 2020

Lecture 24

1

## 1. Differential amplifier: motivation

Remember MOSFET amplifier:

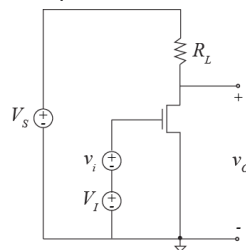

Signal at output under small-signal approximation:

$$\begin{aligned}v_o &= V_O + v_o \\ &\simeq V_S - \frac{KR_L}{2}(V_I - V_T)^2 - KR_L(V_I - V_T)v_i\end{aligned}$$

Output signal depends on:

- power supply and signal bias
- input signal.


6.002 Spring 2020

Lecture 24

2

In circuits, there is often:

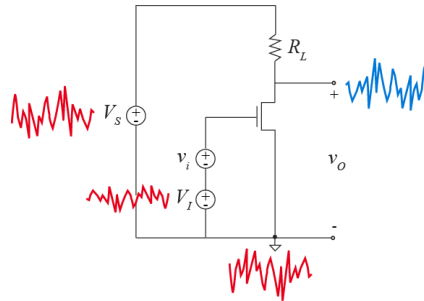- power supply noise and ground noise (cross talk between metal lines, 60 Hz coupling, Si substrate noise)
- Signal bias is often also noisy



Consequence: noisy output!


→ signal can be lost

$$v_o = V_O + v_o$$

$$\simeq V_S - \frac{KR_L}{2}(V_I - V_T)^2 - KR_L(V_I - V_T)v_i$$


Solution:

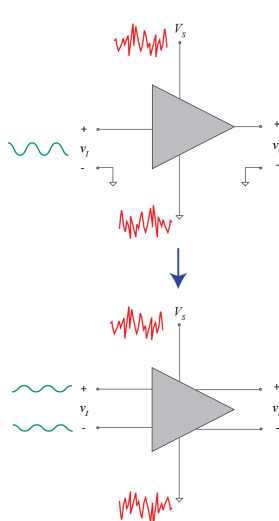- Instead of representing signal by a voltage referred to a fixed reference voltage
- represent signal by the *difference* between two voltages




Develop a *differential amplifier* that:

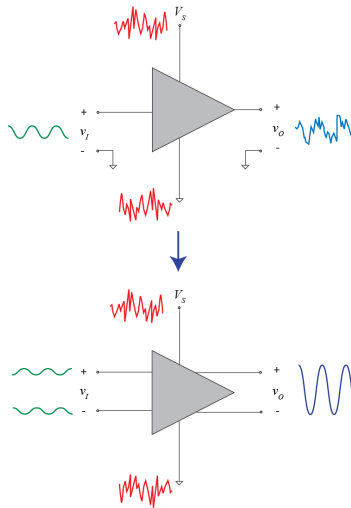- amplifies voltage *difference* between two inputs
- rejects voltage component *common* to both inputs




## 2. MOSFET differential amplifier

Consider the following circuit:

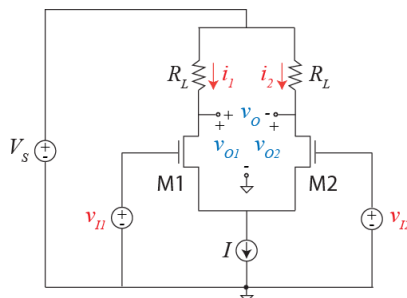

$v_O$  responds to difference of  $v_I$ 's:

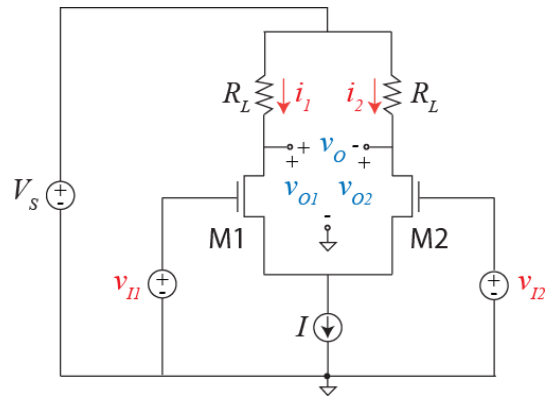- If  $v_{I1} = v_{I2} \rightarrow$  symmetry  
 $\rightarrow v_{O1} = v_{O2} \rightarrow v_O = 0$
- If  $v_{I1} > v_{I2} \rightarrow$  M1 more ON than M2  $\rightarrow i_1 > i_2$   
 $\rightarrow v_{O1} < v_{O2} \rightarrow v_O < 0$
- If  $v_{I1} < v_{I2} \rightarrow$  M1 less ON than M2  $\rightarrow i_1 < i_2$   
 $\rightarrow v_{O1} > v_{O2} \rightarrow v_O > 0$




$v_O$  insensitive to *common mode* of  $v_I$ :

- If noise in common mode of  $v_{I1}$  and  $v_{I2}$   
 → symmetry preserved →  $v_O$  unchanged
- If ground or  $V_S$  have noise, symmetry preserved  
 →  $v_O$  unchanged

Need precise device matching

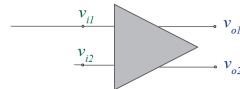In small-signal regime, define differential-mode vs. common-mode signals:



Differential amplifier inputs:

$$v_{i1} = v_{ic} + \frac{v_{id}}{2} \quad v_{i2} = v_{ic} - \frac{v_{id}}{2}$$

Then:


$$v_{id} = v_{i1} - v_{i2} \quad v_{ic} = \frac{v_{i1} + v_{i2}}{2}$$

Similarly at output:

$$v_{o1} = v_{oc} + \frac{v_{od}}{2} \quad v_{o2} = v_{oc} - \frac{v_{od}}{2}$$

And:
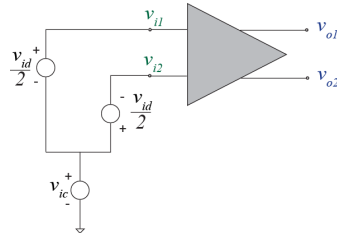
$$v_{od} = v_{o1} - v_{o2} \quad v_{oc} = \frac{v_{o1} + v_{o2}}{2}$$



Figures of merit of interest:

- Differential-mode gain (want high):

$$G_d = \frac{v_{od}}{v_{id}}$$

- Common-mode gain (want small)



$$G_c = \frac{v_{oc}}{v_{ic}}$$

- Common-mode rejection ratio (want high):

$$CMRR = \frac{G_d}{G_c}$$

*Let's calculate all these important parameters!!*

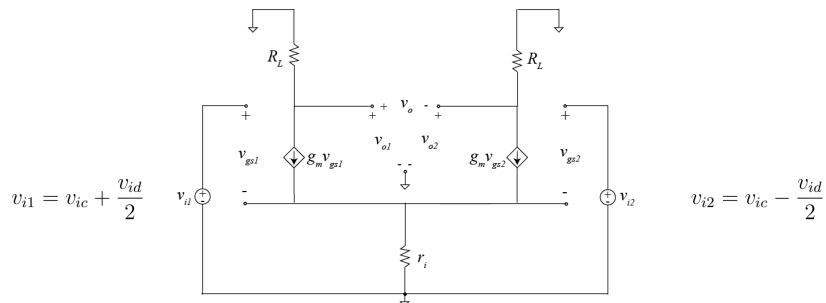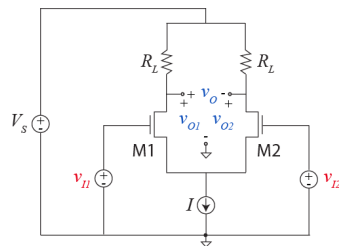
### Small-signal equivalent circuit for MOSFET differential amp



- Differential-mode gain:

$$v_{o1} = -g_m R_L v_{gs1}$$

$$v_{o2} = -g_m R_L v_{gs2}$$

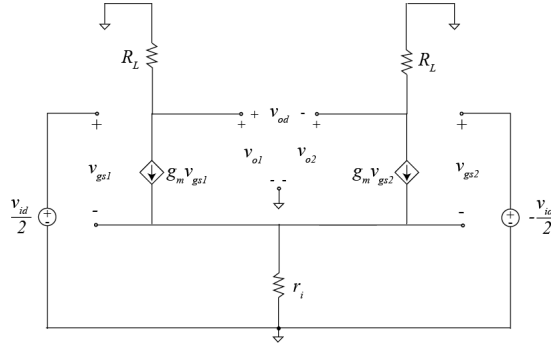

Source of M1, M2 is "incremental ground" and, therefore,

$$v_{gs1} = \frac{v_{id}}{2} \quad v_{gs2} = \frac{-v_{id}}{2}$$

Then:

$$v_{od} = v_{o1} - v_{o2} = -g_m R_L \frac{v_{id}}{2} + g_m R_L \left( \frac{-v_{id}}{2} \right) = -g_m R_L v_{id}$$

Differential gain:

$$G_d = \frac{v_{od}}{v_{id}} = -g_m R_L$$


6.002 Spring 2020

14

- Common-mode gain:

$$v_{o1} = -g_m R_L v_{gs1}$$

$$v_{o2} = -g_m R_L v_{gs2}$$

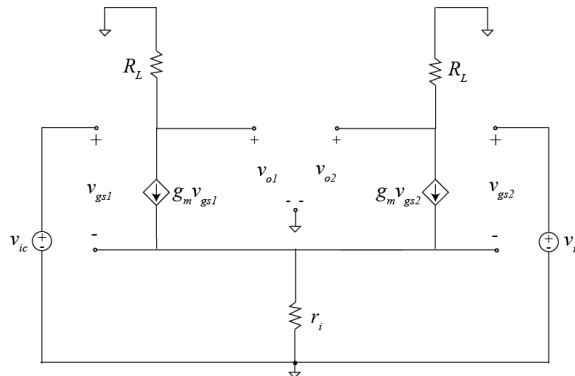

By symmetry:

$$v_{gs1} = v_{gs2} \rightarrow v_{o1} = v_{o2}$$


Common-mode output:

$$v_{oc} = \frac{1}{2}(v_{o1} + v_{o2}) = v_{o1}$$

6.002 Spring 2020

Lecture 24

15

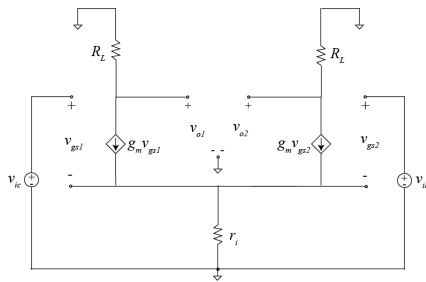

KVL at input:

$$v_{ic} = v_{gs1} + (g_m v_{gs1} + g_m v_{gs2}) r_i = (1 + 2g_m r_i) v_{gs1}$$

Then:

$$v_{gs1} = \frac{v_{ic}}{1 + 2g_m r_i}$$

And:

$$v_{oc} = v_{o1} = -g_m R_L v_{gs1} = -\frac{g_m R_L}{1 + 2g_m r_i} v_{ic}$$


Common-mode gain:

$$G_c = \frac{v_{oc}}{v_{ic}} = -\frac{g_m R_L}{1 + 2g_m r_i}$$

- Common-mode rejection:

$$CMRR = \frac{G_d}{G_c} = 1 + 2g_m r_i$$

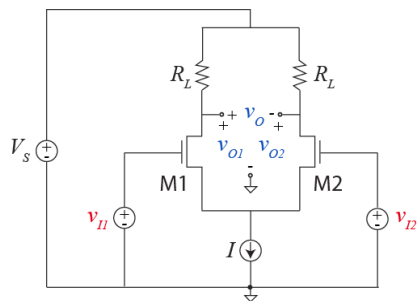Key for common-mode rejection: use a good current source with high  $r_i$




The higher  $r_i$ , the smaller the change in  $I$  as a result of a common-mode signal  
 → the smaller the change in  $v_{o1}$  and  $v_{o2}$
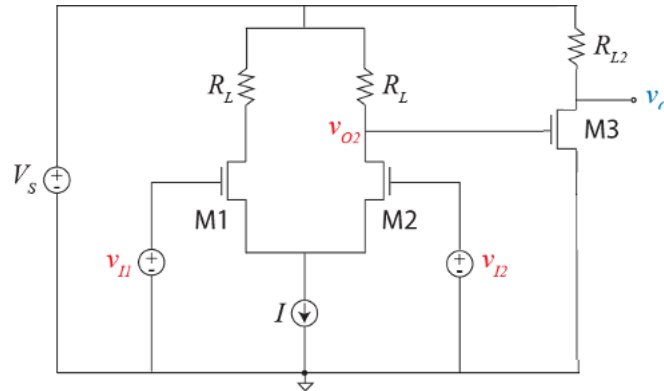
## Towards an operational amplifier

Add “single-ended” MOSFET amplifier at output:


- more gain
- single-ended output
- can design to get  $v_o = 0$  when  $v_{i1} = v_{i2}$



6.002 Spring 2020

Lecture 24

18

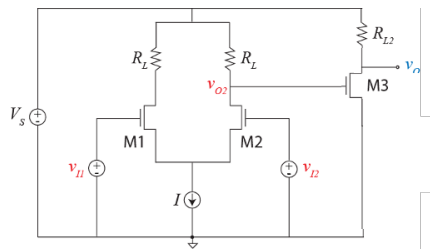

“Single-ended” gain expressed in terms of differential and common-mode gains:

$$\begin{aligned}
 v_{o2} &= v_{oc} - \frac{v_{od}}{2} = G_c v_{ic} - G_d \frac{v_{id}}{2} \\
 &= G_c \frac{v_{i1} + v_{i2}}{2} - G_d \frac{v_{i1} - v_{i2}}{2} \\
 &= \frac{1}{2}(G_c - G_d)v_{i1} + \frac{1}{2}(G_c + G_d)v_{i2}
 \end{aligned}$$

If  $G_d \gg G_c$ :

$$v_{o2} \simeq -\frac{1}{2}G_d(v_{i1} - v_{i2}) = -\frac{1}{2}G_d v_{id}$$

6.002 Spring 2020


Lecture 24

20


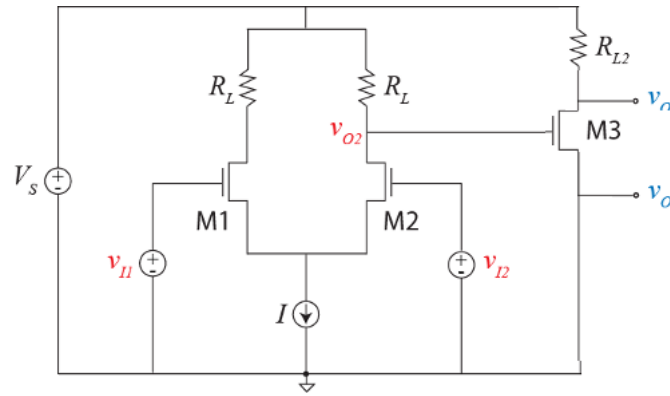
### 3. Amplifier biasing

- How do we apply a small signal on top of a large signal bias voltage?





Many times we want the different stages in our circuit to be independent from each other.

6.002 Spring 2020

Lecture 24

22

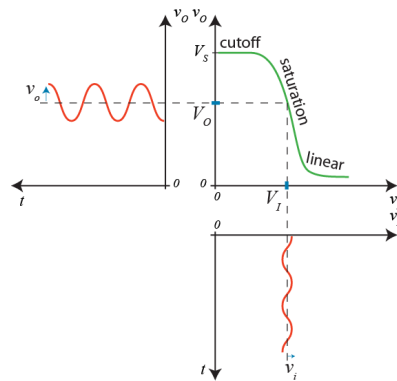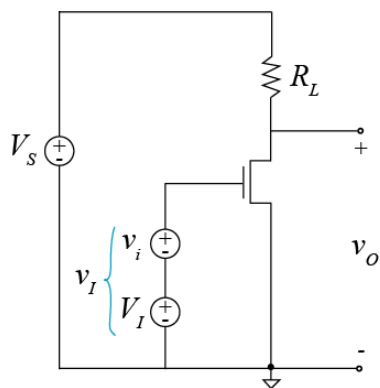- How do we apply a small signal on top of a large signal bias voltage?




6.002 Spring 2020


Lecture 24

23

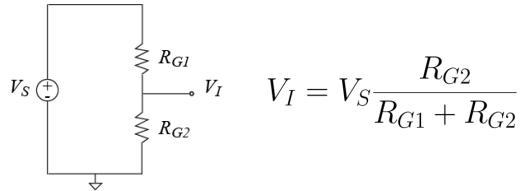
- Problem: need two power supplies,  $V_S$  and  $V_I$
- But, can produce  $V_I$  out of  $V_S$  using voltage divider!



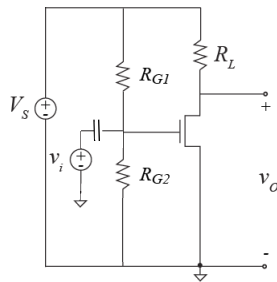- And connecting everything to the circuit:




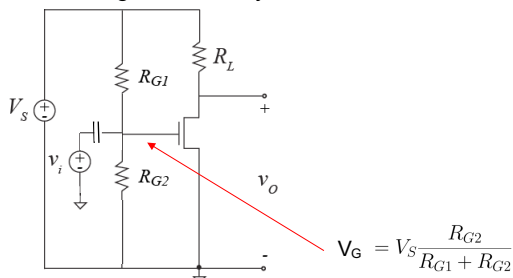- Resistor values have to be designed correctly to bias MOSFET in saturation



input bias too low

input bias too high

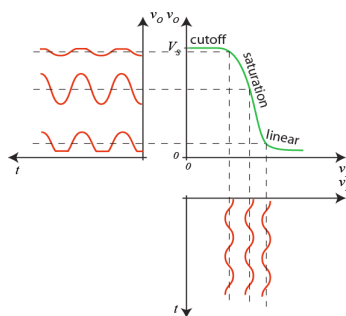

## Summary

- Differential amplifier:
  - amplifies voltage difference between two inputs,
  - rejects voltage common to both inputs
  - achieves greater noise immunity.
- Differential amplifier exploits symmetry: need good matching between components
- In MOSFET differential amplifier, to achieve high common-mode rejection, need high quality current source with very high internal resistance

## Key lessons from 6.002

- Learned basics of analog, logic and power circuits with various devices:
  - Active and passive devices
  - Dissipative and energy storage devices
  - Linear and non-linear devices
- Learned various techniques to analyze circuits depending on the situation
- Learned to think and work in the frequency domain
  - Concept of impedance
- Useful concepts sprinkled along the way:
  - Modular design
  - Noise immunity
  - Concern for power consumption
  - Concern for device variations and matching
  - Temperature stability
- Gained appreciation for the power of math:
  - Complex algebra
  - Differential equations
- Cannot go very far without detailed physical understanding
  
- These are all lessons that go much beyond EE
  - big lessons for engineering

## What comes after 6.002?

6.003: Signals and Systems

- Fundamentals of signal and system analysis

6.012: Microelectronic Devices and Circuits

- Semiconductor device physics, microelectronic circuit analysis and design

6.101: Introductory Analog Electronics Laboratory

6.111: Introductory Digital Systems Laboratory

6.115: Microcomputer Project Laboratory

6.131: Power Electronics Laboratory

6.301: Solid-State Circuits

6.302: Feedback Systems

6.334: Power Electronics

6.374: Analysis and Design of Digital Integrated Circuits

## Good luck with everything!!!

(and let me know if you are interested in a UROP/SuperUROP project  
and/or helping with the VLSI 2020 conference!)